

ADC error solution in WiFi ESP8266

The analog digital convertor's documentation of the ESP8266 circuit is poor and unprecisely. We've observed these problems doing our first experiments with the ESP-12 module.

The documentation is suggesting the analog reference **Aref** is **exactly 1,0V**. There must be 1024 analog to digital conversion steps when aplying 1,0V at the ADC input.


Our experiments show something else !

In reality, **Aref** \neq 1,0V, varying from module to module. The conversion steps number are not equal with the design requirements. These errors cannot be accepted.

Note 1: Until **2.3.0** ESP8266 library version, **Aref** $>$ 1V, the centered value = 1,07V.
 The **2.4.0 - rc2** version makes **Aref** $<$ 1V, the centered value = 0,97V, 100mV less.
 The new centered value is near close to the ideal 1,0V, but **the error is still existing**.

This tutorial helps the users having the same problem.

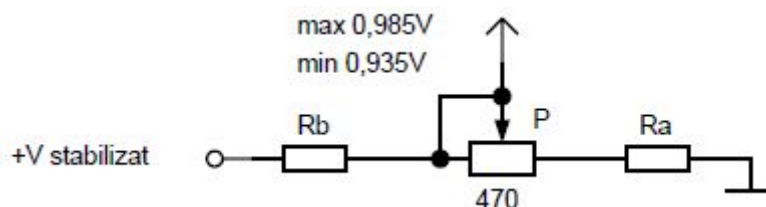Our solution is based on the **Aref** experimental determination value for each ESP-12 module.




Starting from the **+V stabilised** voltage value you have, dimension the divisor so that when turning the **P** potentiometer, the slider voltage value to be included between 0,935~0,985V.

Upload the [check_analog_ref.ino](#) programm and solder the **P** slider to the ADC / ESP-12 input.

Rotate the potentiometer until the **Nadc** steps number printed on the serial Arduino monitor fit 1023~1024 limit. The **P** slider's measured voltage is the **Aref** analog reference value. Write this value on the ESP-12 module. You'll need it!
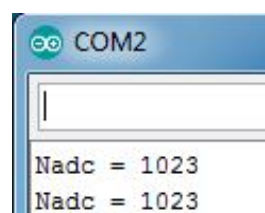
```
void loop() {
  int Nadc = analogRead(A0);
  Serial.print("Nadc = ");
  Serial.println(Nadc);
  delay(1000);
}
```




The ambient temperature measured with the KTY81-210 transducer

We measure the ambient temperature in the $-40 \sim +40$ °C range, precisely, cheap and efficient:

- The **KTY81-210** transducer is a thermistor. The transfer function linearity is done by the help of the serial **R0** resistor
- The transducer may be placed at max 50m distance with a twin braid $2 \times 0,75 \text{mm}^2$ wire.

The KTY81-210 transducer equations

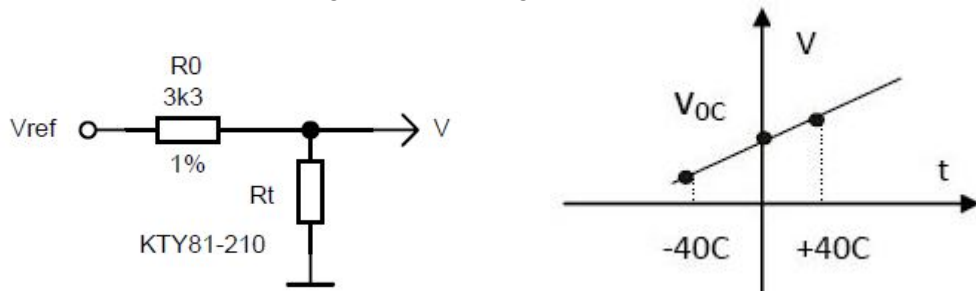
The **R0** = 3300Ω value is providing a very good output voltage **V** linearity depending on **t** temperature and not depending on **Vref** voltage.



$$V = V_{ref} \frac{R_t}{R_t + R_0} \quad (1)$$

choose **Vref** = 2,5V.

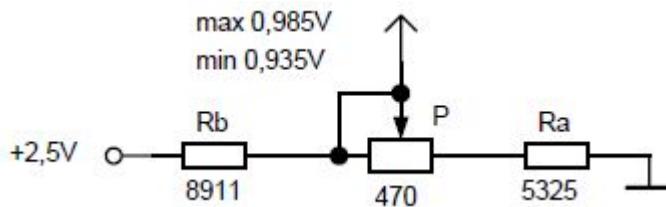The designed divisor to measure the ESP-12 analog reference **Aref** value is:



The **Ra** and **Rb** values result from calculations when **P** = 470Ω , but the **P** tolerance is 20%. The exactly **Ra** and **Rb** values are calculated using the **P** measured value:

- **Ra** = $11,33 \times P$
- **Rb** = $18,96 \times P$

The **Ra** and **Rb** values are done by serial pieces to fit the values.

The KTY81-210 catalog paper show the **Rt** values at various temperatures:

- 1630Ω at 0°C
- 1135Ω at -40°C
- 2245Ω at $+40^\circ \text{C}$
- 2417Ω at $+50^\circ \text{C}$
-

The transducer's output voltage **V** may be written as a strait line depending on the temperature **t**:

$$V = \alpha * t + V_{0C} \quad (2)$$

The V_{oc} and α numerical values are resulting from the equation (1).


$$V_{0C} = 2,5 * \frac{1630}{1630 + 3300} = 0,826572V$$

$$V_{-40C} = 2,5 * \frac{1135}{1135 + 3300} = 0,639797V$$

$$V_{+40C} = 2,5 * \frac{2245}{2245 + 3300} = 1,0121731V$$

$$\alpha = \frac{V_{+40C} - V_{-40C}}{40C - (-40C)} = \frac{1,0121731 - 0,638797}{80} = 4,6547 * 10^{-3} V / ^\circ C$$

The electronic design is:

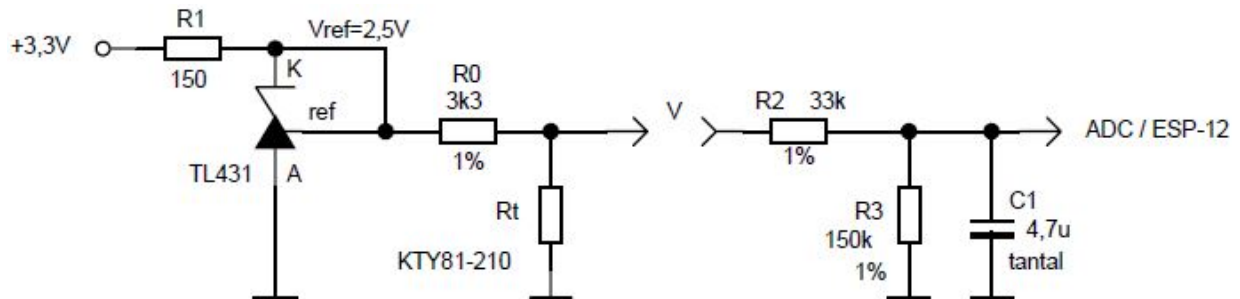

The $R2$, $R3$ divisor drops the V transducer's delivered value to fit the ADC / ESP-12 input range.

The ESP-12 ADC input is converting the divisor's voltage into $Nadc$ steps number depending on the experimental obtained $Aref$ voltage value.

$$V * \frac{R3}{R2 + R3} = Nadc * \frac{Aref}{1024} \quad (3) \quad \text{replace } R_a, R_b \text{ values and send to the right}$$

$$V = Nadc * \frac{Aref}{1024} * \frac{183}{150} \quad (4)$$

Eliminate the V variable in the equations (4) and (2):

$$\alpha * t + V_{0C} = Nadc * \frac{Aref}{1024} * \frac{183}{150}$$

Extract the t temperature and replace α and V_{oc} with their above calculated values:

$$t = Nadc * \frac{Aref}{1024} * \frac{183}{150} * \frac{1000}{4,6547} - \frac{826,572}{4,6547} \quad (5)$$

Amplify the equation with 10.000 and finally divide it only with 1.000:

$$t * 10 = \frac{Nadc * \frac{(Aref * 10000)}{1024} * \frac{183}{150} * \frac{1000}{4,6547} - \frac{8265720}{4,6547}}{1000}$$

do some partial calculations:

$$t * 10 = \frac{Nadc * Aref * 1830000}{714961,92} - 1776 \quad (6)$$


Our ESP-12 exemplar has **Aref = 0,9716V**, experimentaly obtained.

Replace **Aref** value in (6), do the **Aref x 1830000** multiplication and round the integer values:

$$t * 10 = \frac{Nadc * 1777845}{714962} - 1776 \quad (7)$$

Write the equation (7) in the [adc_kty81_210.ino](#) programm. The programm is printing the signed integer part, the decimal comma and the first decimal of the measured temperature:
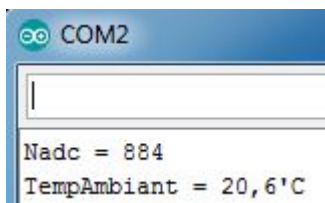
```
Serial.print("TempAmbiant = ");
Serial.print(TempAmbiant/10);           //temperatura in valoare intreaga si semn
Serial.print(",");                       //virgula zecimala
Serial.print(abs(TempAmbiant)%10);      //valoarea zecimala cu ajutorul functiei modulo 10
Serial.println("'C");
```



Note 2: Our experiments have been done using five ESP-12 samples. The experimental Aref obtained voltages were **0,9756V**, **0,9672V**, **0,9853V**, **0,9715V**, **0,9859V** si **0,9791V**. A 3 ½ digital voltmeter is required.

Note 3: We've avoided the float arithmetics operations. The measured resolution is ~ 0,3 °C.

Run also the [adc_kty81_210_isr.ino](#) and [web_kty81_210.ino](#) examples.

The WiFi ESP-12 [test board](#) and accesories

